

Project 5: Computer Architecture - Building the Hack Computer

Overview

In Project 5 of the Nand to Tetris course, we culminate our journey from basic logic gates to constructing a complete, functional computer. This project integrates all the components we've built in previous projects:

- **Logic Gates** (Project 1): Basic building blocks
- **ALU (Arithmetic Logic Unit)** (Project 2): Performs arithmetic and logical operations
- **Memory** (Project 3): RAM hierarchy and registers
- **Assembler** (Project 4): Translates assembly code to machine code

The Hack Computer consists of three main components:

1. **CPU (Central Processing Unit)**: Executes instructions
2. **Memory**: Stores data and instructions
3. **ROM (Read-Only Memory)**: Holds the program to be executed

The Hack Computer Architecture

The Hack Computer is a 16-bit von Neumann architecture machine with the following specifications:

- **Word Size**: 16 bits
- **Address Space**: 15 bits (32,768 addresses)
- **Instruction Set**: Two types - A-instructions and C-instructions
- **Memory Map**:
 - RAM: 0x0000 - 0x3FFF (16K words)
 - Screen: 0x4000 - 0x5FFF (8K words)
 - Keyboard: 0x6000 (1 word)

Computer.hdl - The Top-Level Chip


The [Computer.hdl](#) file represents the complete Hack computer:

```
CHIP Computer {  
    IN reset;  
    PARTS:  
        ROM32K(address=PC, out=instruction);  
        CPU(inM=memOut, instruction=instruction, reset=reset,  
             outM=outM, writeM=writeM, addressM=addressM, pc=PC);  
        Memory(in=outM, load=writeM, address=addressM, out=memOut);  
}
```

- **ROM32K**: Stores the program (32K instructions)
- **CPU**: Executes instructions, interfaces with memory

- **Memory:** Data memory (RAM + Screen + Keyboard)

The CPU (Central Processing Unit) :

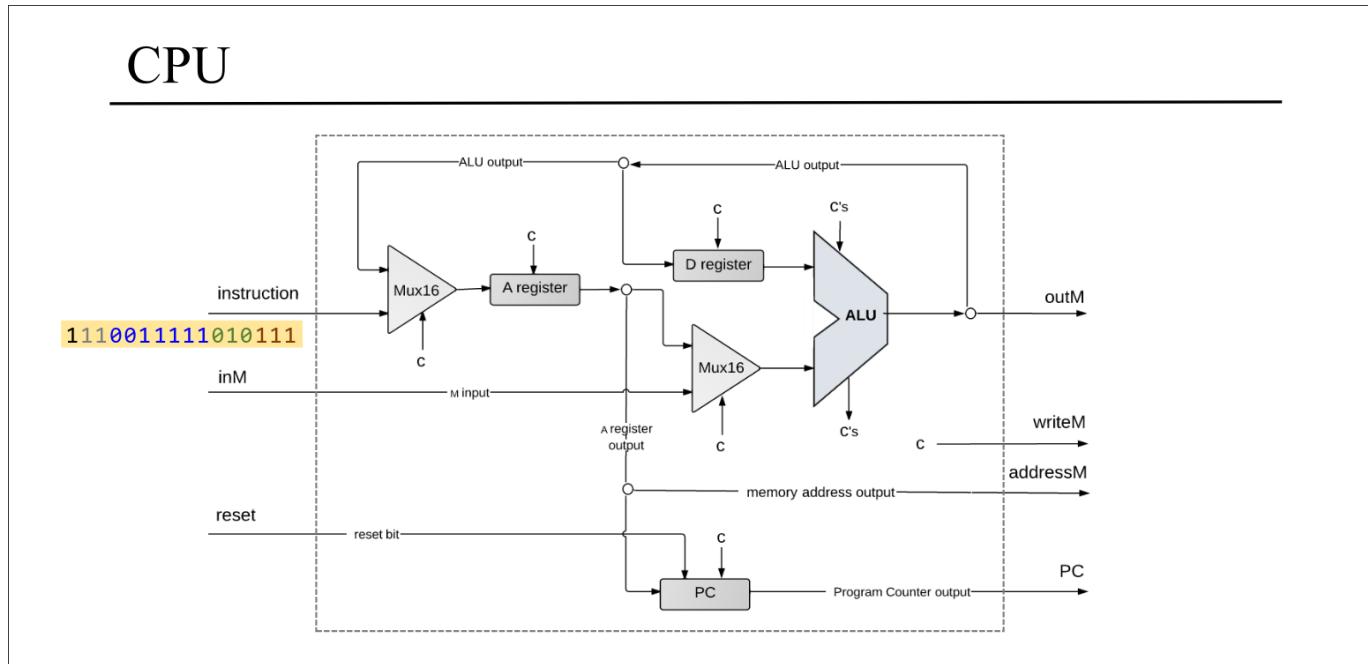

The CPU is the "brain" of the computer, responsible for fetching, decoding, and executing instructions. It contains:

- **A Register:** 16-bit register for addresses/values
- **D Register:** 16-bit register for data
- **ALU:** Performs computations
- **Program Counter (PC):** Points to next instruction

CPU Architecture

The CPU follows a classic von Neumann cycle:

1. **Fetch:** Get instruction from ROM[PC]
2. **Decode:** Determine instruction type and operation
3. **Execute:** Perform the operation
4. **Update PC:** Point to next instruction

Instruction Set Architecture

The Hack ISA has two instruction types:

A-Instructions (Address Instructions)

- Format: 0vvvvvvvvvvvvv (15 bits of address/value)
- Operation: A = vvvvvvvvvvvvv
- Purpose: Load a value into the A register

C-Instructions (Compute Instructions)

- Format: **111accccccdddjjj**
- Fields:
 - **a**: ALU y-input selector (0=A register, 1=Memory[A])
 - **cccccc**: ALU control bits (6 bits)
 - **ddd**: Destination bits (A, D, M registers)
 - **jjj**: Jump condition bits

ALU Operations

The ALU performs 18 different operations based on 6 control bits:

zx	nx	zy	ny	f	no	Operation
1	0	1	0	1	0	0
1	1	1	1	1	1	1
1	1	1	0	1	0	-1
0	0	1	1	0	0	x
1	1	0	0	0	0	y
0	0	1	1	0	1	!x
1	1	0	0	0	1	!y
0	0	1	1	1	1	-x
1	1	0	0	1	1	-y
0	1	1	1	1	1	x+1
1	1	0	1	1	1	y+1
0	0	1	1	1	0	x-1
1	1	0	0	1	0	y-1
0	0	0	0	1	0	x+y
0	1	0	0	1	1	x-y
0	0	0	0	0	0	x&y
0	0	0	0	0	1	x


Jump Conditions

The CPU supports 7 jump conditions based on ALU output flags:

jjj	Condition	Meaning
000	Never	No jump
001	JGT	if out > 0

jjj	Condition	Meaning
010	JEQ	if out = 0
011	JGE	if out \geq 0
100	JLT	if out $<$ 0
101	JNE	if out \neq 0
110	JLE	if out \leq 0
111	JMP	Unconditional

Memory System

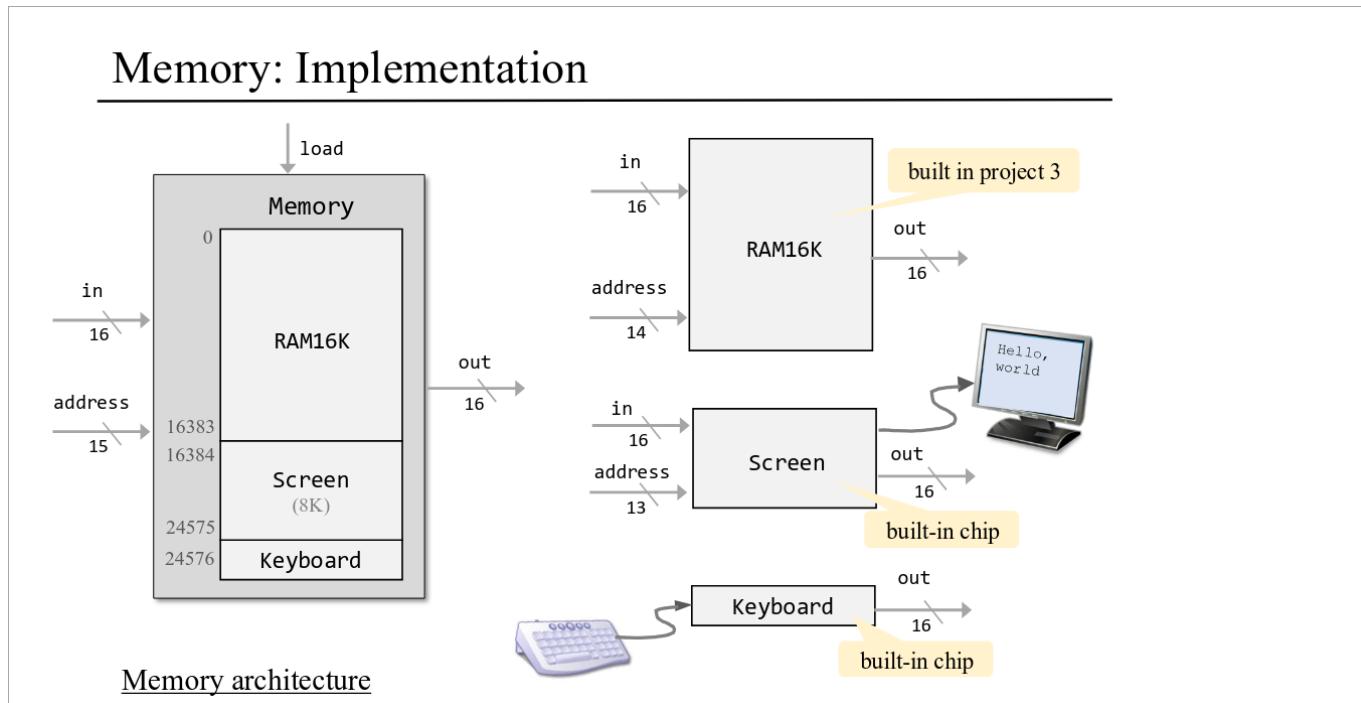

The Hack Computer has a unified memory address space divided into three regions:

RAM16K (Data Memory)

- Address range: 0x0000 - 0x3FFF
- 16,384 words of read/write memory
- Built hierarchically: RAM16K \rightarrow 4xRAM4K \rightarrow 8xRAM512 \rightarrow 8xRAM64 \rightarrow 8xRAM8 \rightarrow 8xRegister

Screen Memory Map

- Address range: 0x4000 - 0x5FFF
- 8,192 words (32,768 pixels)
- Each word represents 16 consecutive pixels
- Writing to screen memory updates the display

Keyboard Memory Map

- Address: 0x6000

- Single word containing ASCII code of pressed key
- Read-only; writing has no effect

Program Execution

The Fetch-Execute Cycle

1. **Fetch:** $\text{instruction} = \text{ROM}[\text{PC}]$
2. **Execute:**
 - If A-instruction: $A = \text{instruction}[14..0]$
 - If C-instruction:
 - Compute: $\text{ALUout} = \text{ALU}(D, A/M, \text{control_bits})$
 - Store results in specified destinations
 - Evaluate jump condition and update PC accordingly
3. **PC Update:** $\text{PC} = \text{PC} + 1$ or jump address

Timing Considerations

- **Combinational Outputs:** outM , writeM change immediately
- **Clocked Outputs:** addressM , pc change on next clock cycle
- Memory writes take effect on the next cycle

Building the Computer

Implementation Details

CPU Implementation ([CPU.hdl](#))

- **Instruction Decoding:** Uses combinational logic to decode instruction bits
- **Register Control:** A and D registers load based on instruction type and destination bits
- **ALU Integration:** ALU output feeds back to registers and memory
- **Jump Logic:** Evaluates ALU flags against jump bits to control PC

Memory Implementation ([Memory.hdl](#))

- **Address Decoding:** Uses $\text{address}[13..14]$ to select memory region
- **DMux4Way:** Routes load signal to appropriate memory component
- **Mux4Way16:** Selects output from the addressed memory region

Key Design Patterns

1. **Hierarchical Design:** Complex chips built from simpler ones
2. **Time-Separation:** Combinational vs. sequential logic
3. **Address Decoding:** Multiplexing/demultiplexing for memory mapping
4. **Control Signals:** Load signals control when data is stored

Testing and Validation

The computer is tested by:

1. Loading machine code programs into ROM32K
2. Running the computer with `reset=1` then `reset=0`
3. Observing memory contents, screen output, and PC progression

Sample Programs

- **Add.hack**: Adds two numbers
- **Max.hack**: Finds maximum of two numbers
- **Rect.hack**: Draws rectangles on screen
- **Pong.hack**: Interactive Pong game

Significance

Project 5 represents the culmination of the Nand to Tetris journey. By building a complete computer from first principles, we've demonstrated:

- How hardware and software interact
- The von Neumann architecture in practice
- The power of abstraction and hierarchical design
- The foundation of modern computing systems

This computer, though simple, can run complex programs including operating systems, compilers, and games - proving that all software is ultimately executed by logic gates manipulating bits.

Further Reading

- "The Elements of Computing Systems" by Nisan and Schocken
- Nand2Tetris website: www.nand2tetris.org
- Computer Organization and Design by Patterson and Hennessy